



# Lab 1 – Preparation

# Reminders


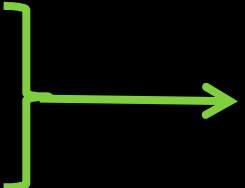
- Labs take place in BA3145, BA3155, BA3165
  - L0101: Wednesdays 6-9pm.
  - L5101: Thursdays 6-9pm.
- Some Rules:
  - These labs are only open and available during your dedicated lab section.
  - You must work in pairs.
  - After your first lab you will be assigned a lab station for the entire term.
  - **No food or drinks permitted in the labs!**
    - Please respect this to protect the lab equipment.
- A brief lab guide:
  - <http://www-ug.eecg.toronto.edu/msl/handouts/labguide.html>
  - Note: some parts apply mainly to engineering students.

# Lab 1 Learning Objectives

- Learn how to build logic circuits by using chips that contain individual logic gates .
- Produce truth tables for a given design (starting either from a given logic function or from a description of the design's behaviour).
- Gain familiarity with the schematic builder tool of Quartus.

# Preparing for Lab 1

- Experience is the best teacher.

- Preparing a design.  Pre-Lab
- Implementing your design.  In-Lab
- Debugging the circuit.

- Try to think of your prelabs as “an assignment due in the beginning of the lab”.



# Equipment

- Breadboard
- Wires
- Gates



 
 
# Breadboard

- The standard working area for connecting digital components together.
- Red and blue horizontal rows at top are connected.
- Columns in middle sections are connected.



  
# Wires

- Use this to connect different components together.
- Use the pre-cut wires whenever possible.
- Learn how to strip the coating off the end of a wire.


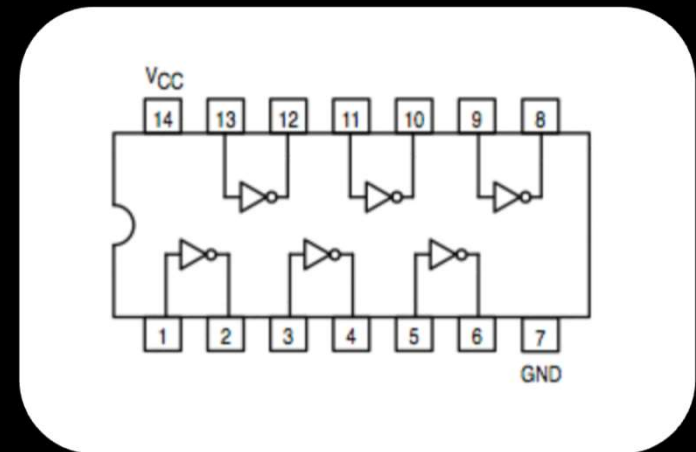
# Gates


- IC chips will be supplied, which house the gates that you will use to create circuits.
- Example: 74LS04 (NOT)
  - Notch at one end helps determine alignment.
  - Usually a dot at pin #1.
  - $V_{CC}$  and GND always have to be connected to the power source and the ground, respectively.






# Other Gates

- 74LS08 (AND)

 

- 74LS32 (OR)

 

# Tips

- Remember to turn off the power supply when connecting/plugging in components in the breadboard.
- Using some sort of colour convention for your wires can be helpful.
  - e.g. have all wires connected to the ground be one colour and use another colour for all  $V_{CC}$  wires.
- Use the logic probe (provided in the lab kit) to test each connection when debugging!

# Pre-lab report

- Should include the following:
  - Lab number and title
  - Student info (last name, first name, student #)
  - Exercise parts
    - Each in its own clearly-labeled section.
    - Restate the question (summarized).
    - Provide the calculations (if applicable).
    - Illustrate the solution (including pin labels).
  - BE NEAT.

# Warm Up Example

- Design a circuit that implements the following logic function, using only 2-input AND and 2-input OR gates.

$$f = ab + (c + b)$$

- Write down the truth table for this design.

## Warm Up Example cont'd

- Is there a cheaper implementation (i.e., with fewer gates)?
  - $f = ab + (c + b)$



# Things to note

- This will be the easiest lab you do in the course.
- Whenever possible, use the tools and bring in a printed pre-lab report.
- Try to come up with the smallest circuits possible.
  - How do you reduce a complex circuit?
  - For now, think back to boolean algebra axioms!
  - Simple reasoning helps as well 😊

# After the lab reflect on

..how long it took you to implement even simple logic circuits on the breadboard.

- Can you imagine doing this for more complex circuits?
  - ▣ Hardware Description Languages (HDL), like **Verilog**, and **design tools** to the rescue! 😊